

**DS20613 - Assignment 4 – Pull Up/Down Resistor**  
**Submitted on 23 October 2020**


**Name:** Theivaprakasham H

**Roll Number:** CB.EN.P2CEN20026

**List of Components**


Name	Quantity	Component
U1	1	Arduino Uno R3
D1	1	White LED
D2	1	Red LED
R1		
R2		
R3		
R4	4	10 k $\Omega$ Resistor
B1		
B2	2	Push Button

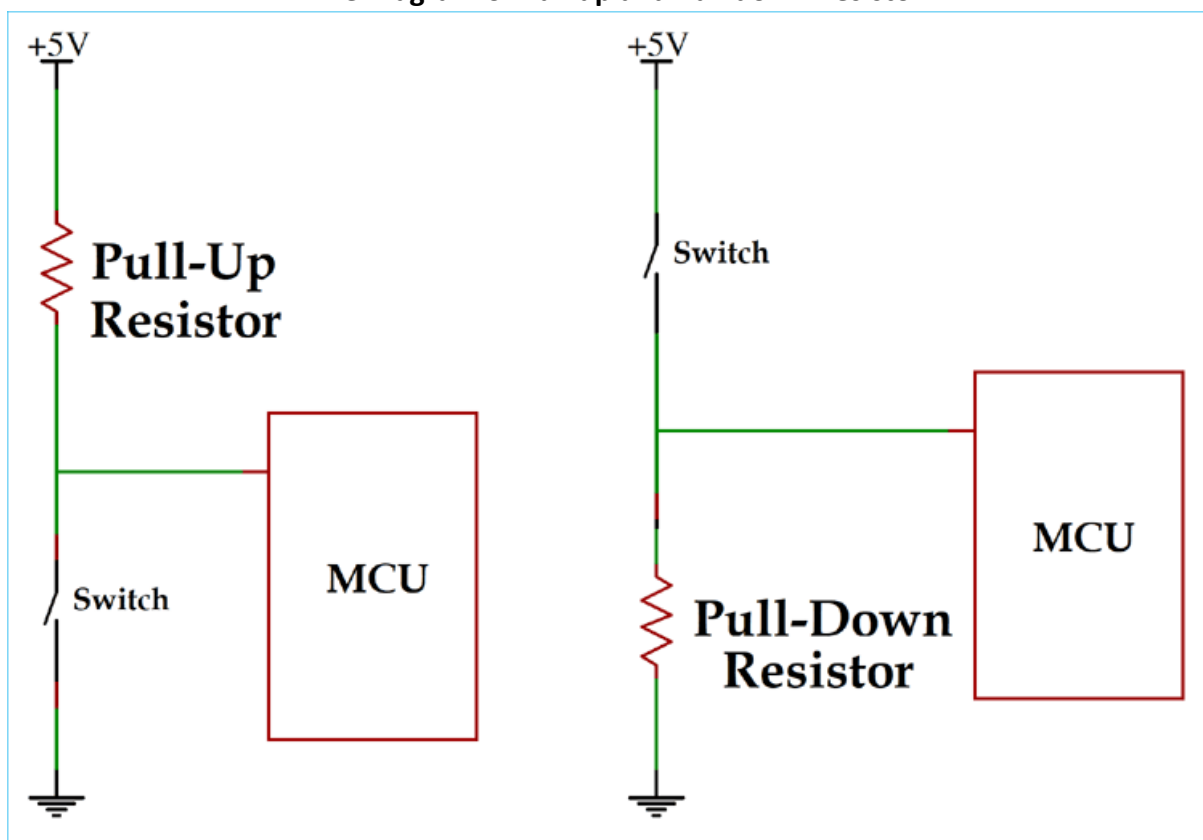**Wire Diagram of Pull up and Pull down Resistor**




\*MCU - Micro Controller Unit

**Breadboard view:**

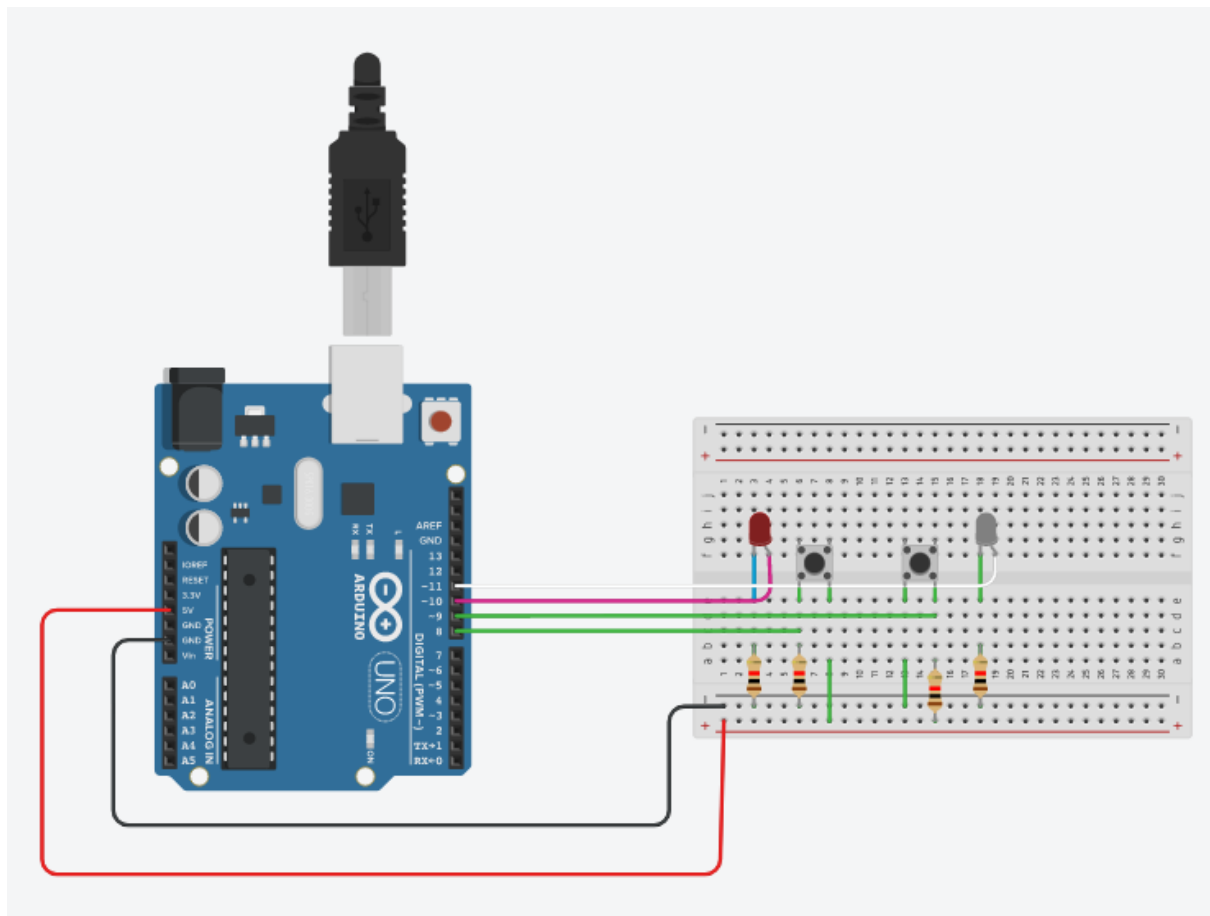


**Live implementation view**

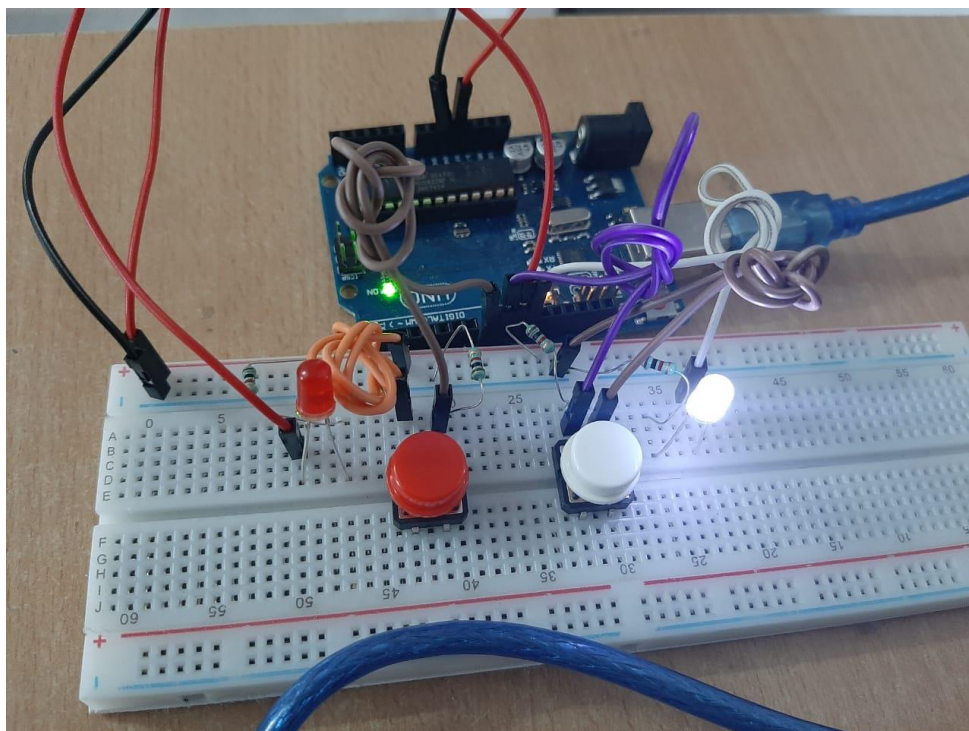


**Pull Up Mode:** In Pull-up configuration, the power source(5V) is connected to the resistor followed by the Digital INPUT pin9 which make the Digital Input value always HIGH. A switch is connected from Digital pin 9 to the ground. Whenever the White Switch is pressed, the voltage at the Digital INPUT Pin 9 will go low as the pin is gets shorted to Ground (0V).

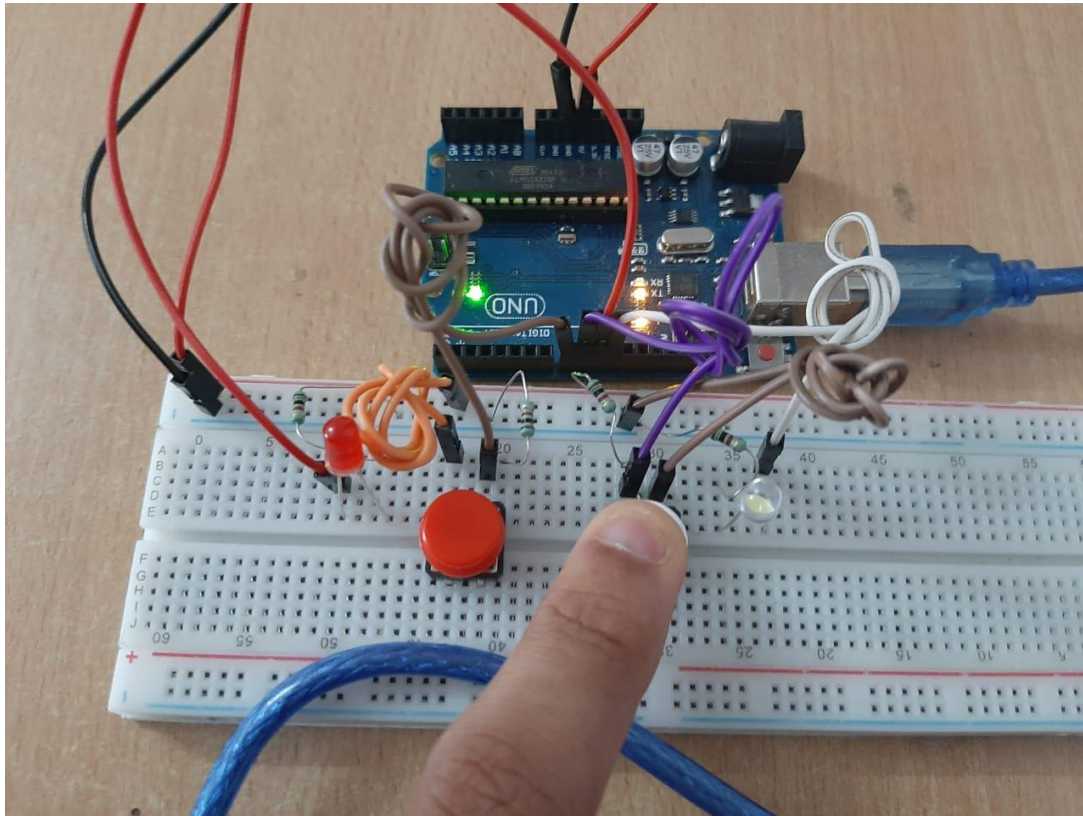In this experiment, we will read the status of Digital INPUT pin 9 and accordingly Power ON/OFF a White LED connected to Digital INPUT pin 11.




### Serial Ouput:

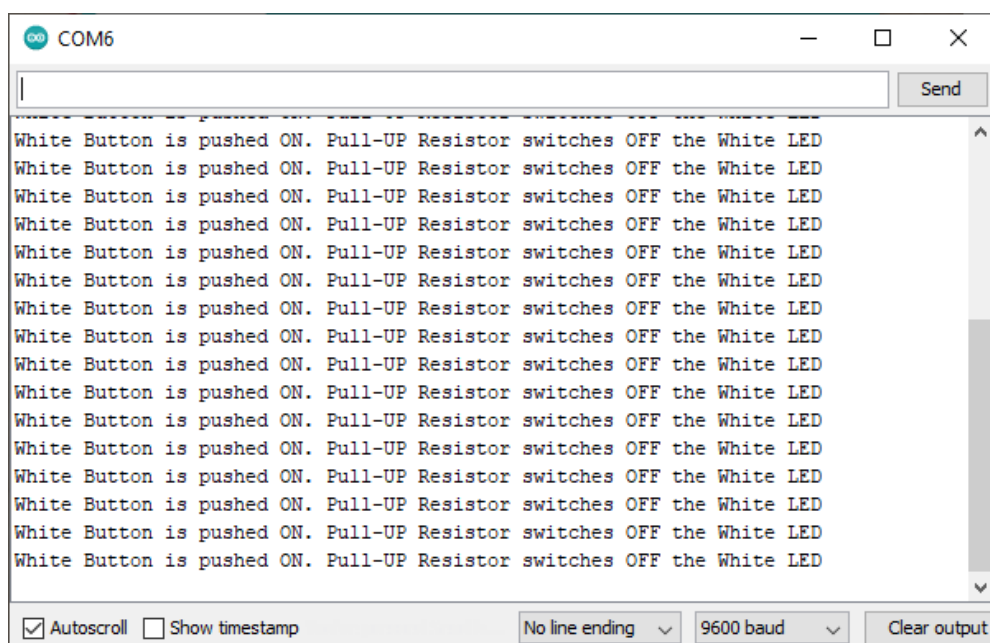


**Pull Down Mode:** In Pull-down configuration, the power source(5V) is connected to the switch followed by the Digital INPUT pin8 which make the Digital Input value always LOW. A resistor is connected from Digital pin 8 to the ground to maintain a reference voltage of 0V in the Digital Pin 8. Whenever the Red Switch is pressed, the voltage at the Digital INPUT Pin 8 will be HIGH as the power source(5V) gets shorted to Digital INPUT Pin 8.

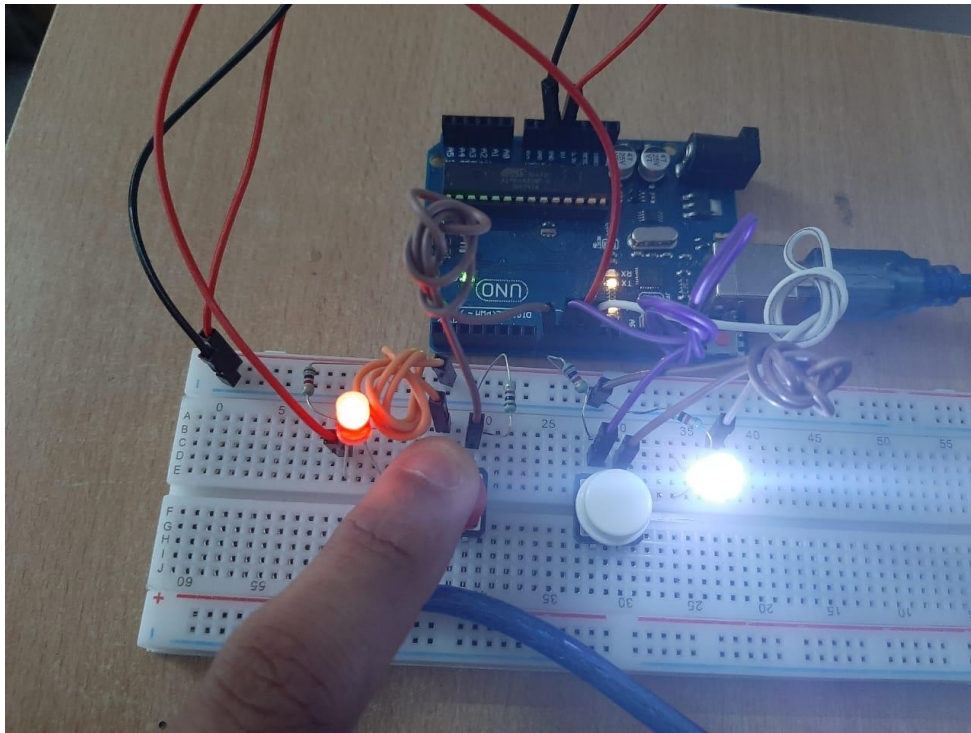In this experiment, we will read the status of Digital INPUT pin 8 and accordingly Power ON/OFF a RED LED connected to Digital INPUT pin 10.



**Serial Ouput:**

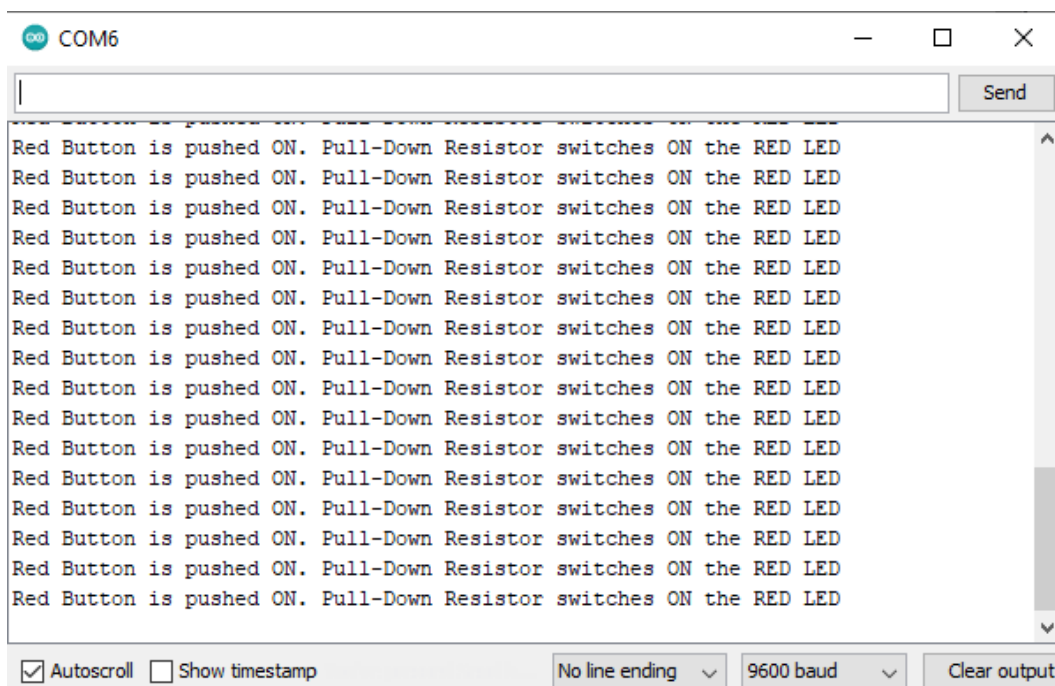

## Code:

```
/*
@author: Theivaprakasham H
@title: Pull Up and Pull Down Resistors with Switch
*/

// Initializing two variables to store the state of the buttons
int buttonState1, buttonState2;

void setup() {
  //start serial connection
  Serial.begin(9600);

  // Setting button1 = D8(Input) ; button2 = D9(Input); RedLed = D10(Output); WhiteLed = D11(Output);
  DDRB = B00001100;
}

void loop() {

  // Read the state of the pushbutton value:
  buttonState1 = PINB & B00000001; //performing AND operation to PINB to extract D8 value
  buttonState2 = PINB & B00000010; //performing AND operation to PINB to extract D9 value


  // Checking the status of Button1
  if (buttonState1 == B00000001) { PORTB = PORTB | B00000100; // turn on Red Led(D10)
    Serial.println("Red Button is pushed ON. Pull-Down Resistor switches ON the RED LED");
  } else {
    PORTB = PORTB & B11111011; // turn RED LED off
  }

  // Checking the status of Button2
  if (buttonState2 == B00000010) { PORTB = PORTB | B00001000; // turn ON White Led(D11)
  } else {
    PORTB = PORTB & B11110111; // turn WHITE LED off
    Serial.println("White Button is pushed ON. Pull-UP Resistor switches OFF the White LED");
  }
}
```